

# EE-577B Project - Phase 2

## Gold Variable-Width Processor

Andrew Adam  
Harsh Bhardwaj

# Agenda

- Overview of design
  - Division of work
- Processor Pipeline
  - Register File
  - Stalling
  - Forwarding
  - Branches
- ALU
  - Shifters
  - Multipliers
- Testing & Synthesis
- Q & A

# Overview

- Four-stage variable-width processor

- Flow

- Design → RTL → Testing → Synthesis

- Division of work

- Andrew

- Logical & Shift instructions

- Memory instructions

- Register file

- Program counter

- Harsh

- Arithmetic instructions

- Branch instructions


- Perl compiler script

- Both

- Pipeline structure and components


- ALU structure

# High-level Block Diagram

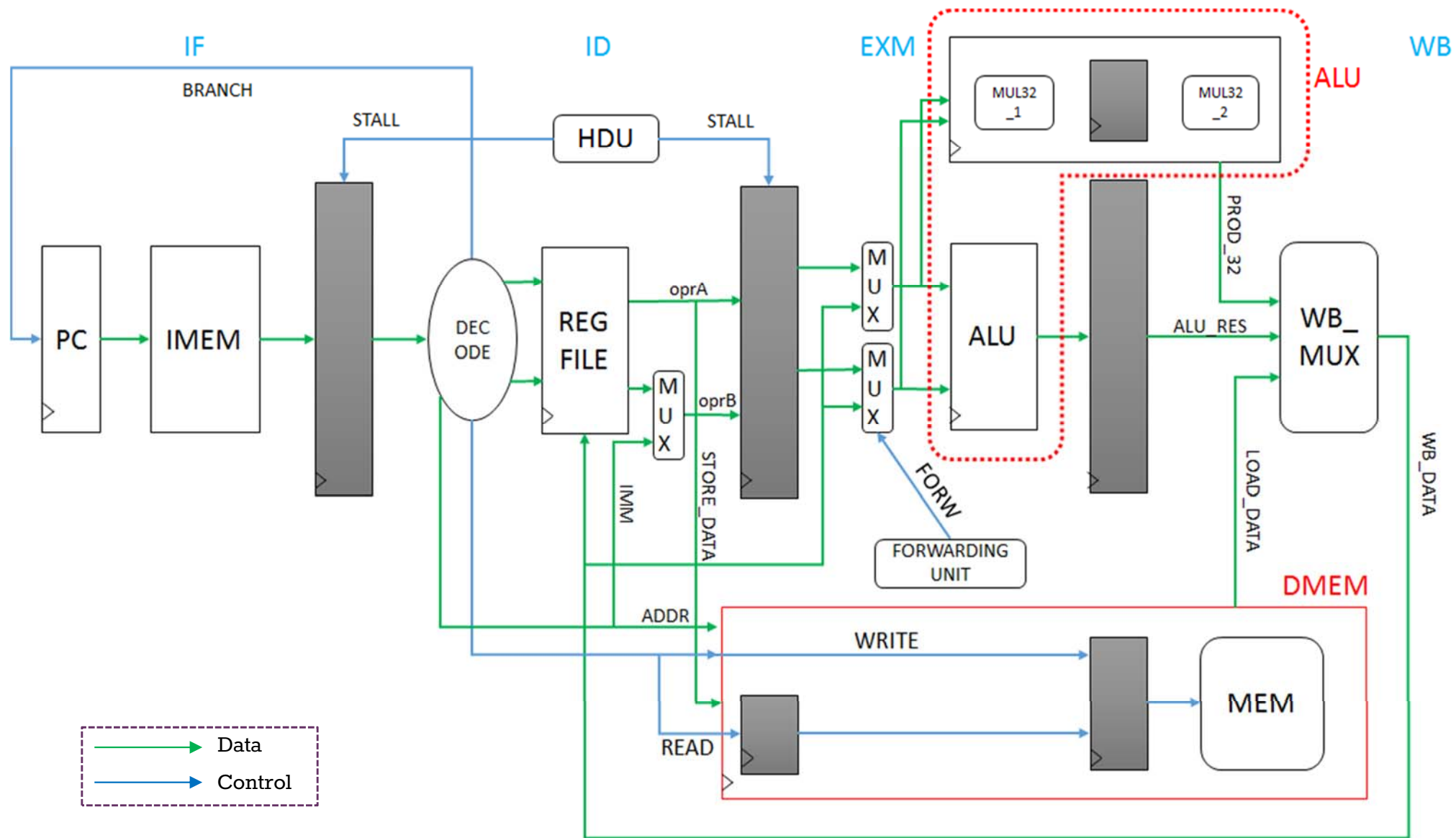

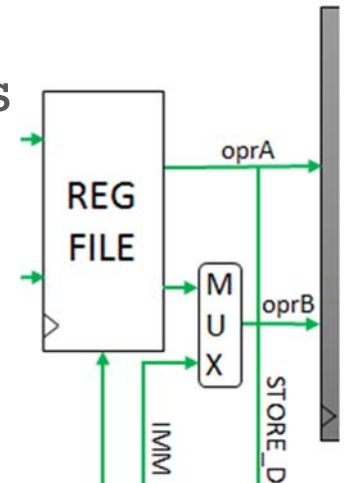
# Processor Pipeline - Register File

- Tradeoff between 1-D [width\*depth] vs 2-D reg file [width][depth]
- Key Features:
  - Internally forward if write address = read address
  - Participation fields used in reg file
    - 1) Ex stage calculation assumes all fields participate
    - 2) Reg file - get value of current reg file
    - 3) Calculate what to write back based on new write data, current reg, and PPP
  - Each instruction therefore takes 1 cycle for execution (2 cycles for multiply)



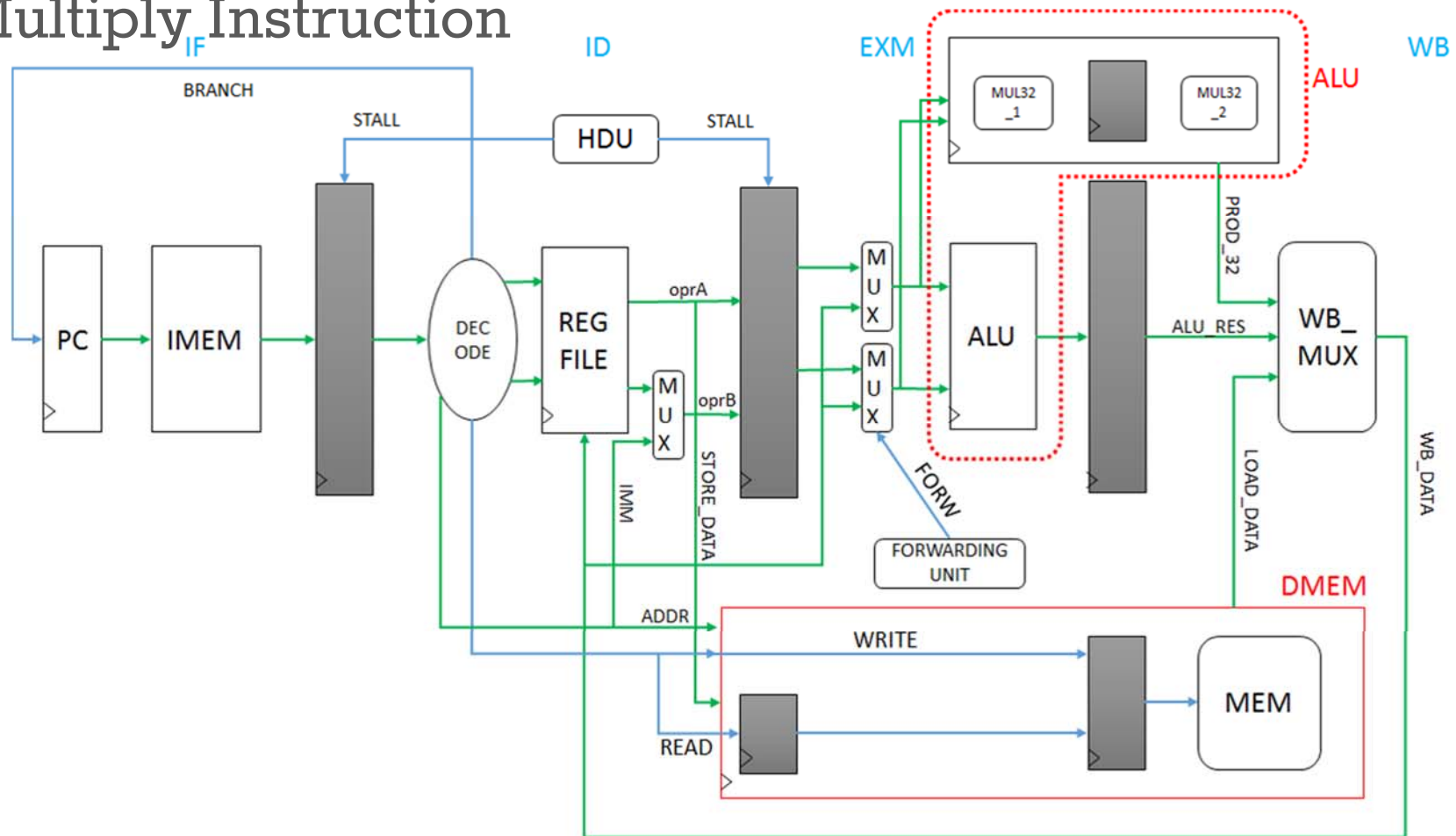
# Processor Pipeline - Stalling

- Store Instruction
- Branch Instruction
- Multiply Instruction



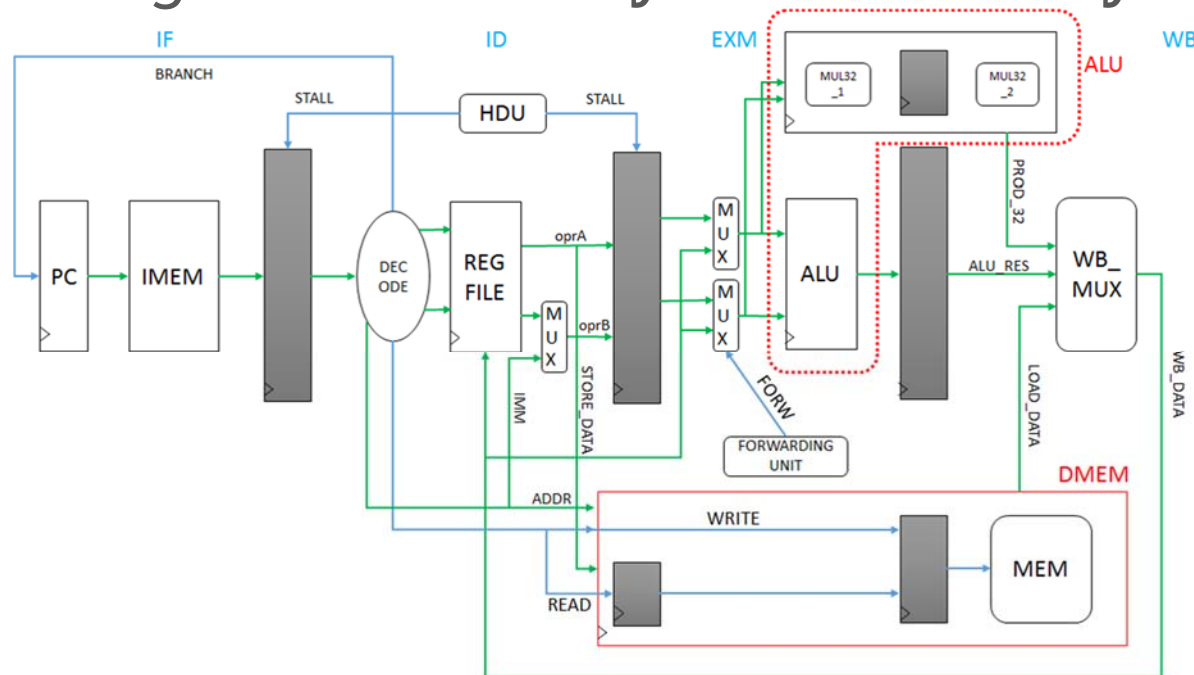
# Processor Pipeline - Forwarding

- Forward according to PPP value when:
  - Write back stage destination register file = EX stage stage destination register file
  - Register write is enabled in both EX and WB stages
  - Applies for both R-type and Load instructions
- When stalling - forward only on 1st clock cycle of stall


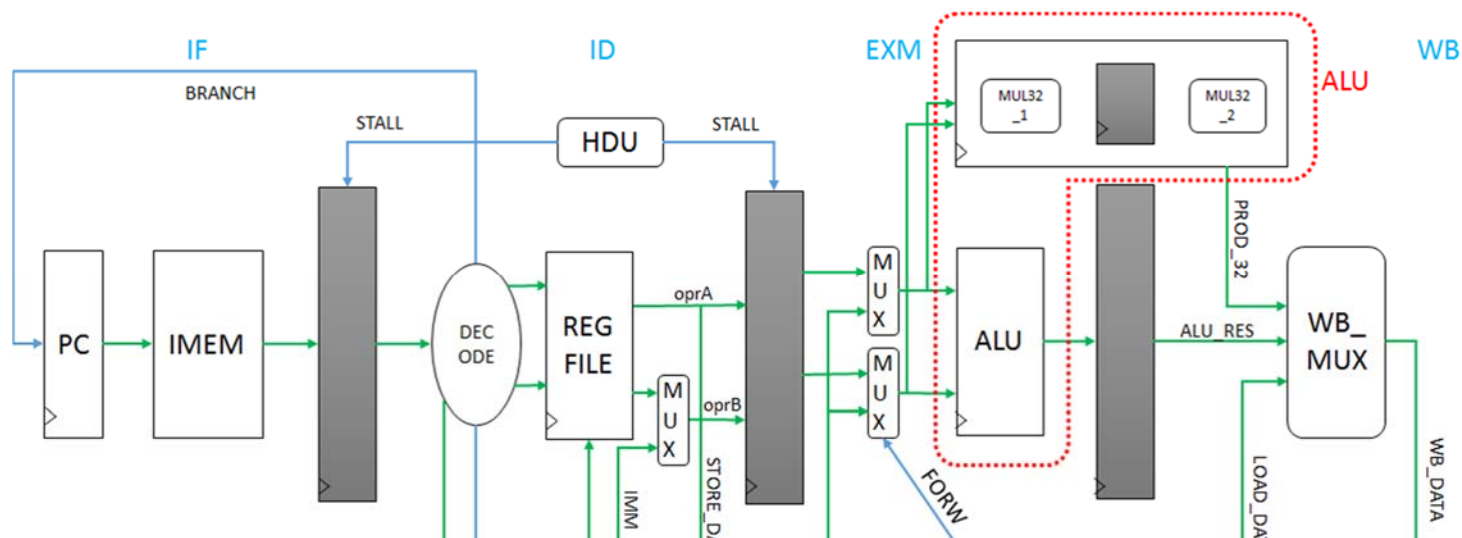
# Processor Pipeline - Branches


- ID stages includes a comparator
  - Determines if the register file address read is zero or not zero
- The result of this ID branch signal is used to load the PC if stall is not active
- If current branch in ID stage is successful, tag the instruction in IF stage to be flushed




 
# ALU

- Logical Operations
  - AND, OR, XOR, NOT, MOV
- Arithmetic Operations
  - ADD, SUB
  - Multiplication
- Shift Operations
  - Rotate
  - Logical Shift
  - Arithmetic Shift
- WW field determines operand width
  - Not considered for logical operations
- Two-cycles for 32-bit multiplication
  - One-cycle operation for all other instructions



# ALU - Shifters

## ■ Logical Shifting

- Left- and right-shift
- Eight 8-bit shifters
- Four 16-bit shifters
- Two 32-bit shifters
- One 64-bit shifter

## ■ Arithmetic Shifting

- Only right-shift

## ■ Shift amount - Immediate or register-value

## ■ Coding style for arithmetic-shifting

### ■ \$signed

- Type-cast function
- Sign-extension
- Synthesizable


### ■ “>>>”

- Verilog arithmetic right-shift operator


■ `result = $signed(oprA) >>> oprB[58:63];`
 
# ALU - Multipliers

- 8-bit Multipliers
  - Four 8x8 multipliers
  - Byte multiplication
- 16-bit Multipliers
  - Two 16x16 multipliers
  - Halfword multiplication
- 32-bit Multiplier
  - Word multiplication
  - One 2-stage pipelined DesignWare multiplier instance
    - DW02\_mult\_2\_stage
    - Implementation - Booth-recoded Wallace-tree
- Even and Odd multiplication
- Square Operations



 (a) Before pipeline retiming  
(before compile)



(b) After pipeline retiming  
(after compile)

Fig. - DW02\_mult\_2\_stage block diagram  
(source - Synopsys DesignWare document library)

# Testing & Synthesis

## ■ Test methodology

- Write assembly code
- Perl script to convert to binary
- Observe waveforms and DMEM dump file
- Separate test-benches for register-file, ALU
- Test-cases
  - ALU operations
  - Load and Store
  - Branches
  - Stalling & Forwarding

## ■ Synthesis

- Meets 4 ns clock-period requirement
- 2.4 ns cycle time possible too!
- `report_resources` command

# Q & A